


# Proiect CID

Goia Calin-Daniel

gr.2124 sg1
 
## Rezolvare pe hartie:

Să se proiecteze automatul de transfer 8 folosind un numărator pe 4-biți, decodificatorul de adresă D și un multiplexor IV.



D.

D	clk	ld	en	Action
0	x	x	x	Reset
1	↓	1	x	Load
1	↓	0	0	Count
otherwise				Wait

IV. MUX 4:1 și MUX 2:1

G <sub>2</sub>	G <sub>1</sub>	G <sub>0</sub>	Ld	En	C B A		
					D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>
0	0	0	1	x	1	0	0
0	0	1	1	x	0	0	0
0	1	0	x	x	x	x	x
0	1	1	1	x	0	0	1
1	0	0	1	x	1	1	0
1	0	1	x	x	x	x	x
1	1	0	0	0	x	x	x
1	1	1	1	x	0	1	1

$Q_2 \backslash Q_1 Q_0$	00	01	11	10
0	1	x		1
1	1	1	1	x


$$Ld = \bar{Q}_1 + Q_0 Q_1$$

$$Em = '0'$$

$$D_2 = \bar{Q}_0$$


$$D_1 = Q_2$$

$$D_0 = Q_1$$

 


## Sursele de proiectare:

Mux2:1:

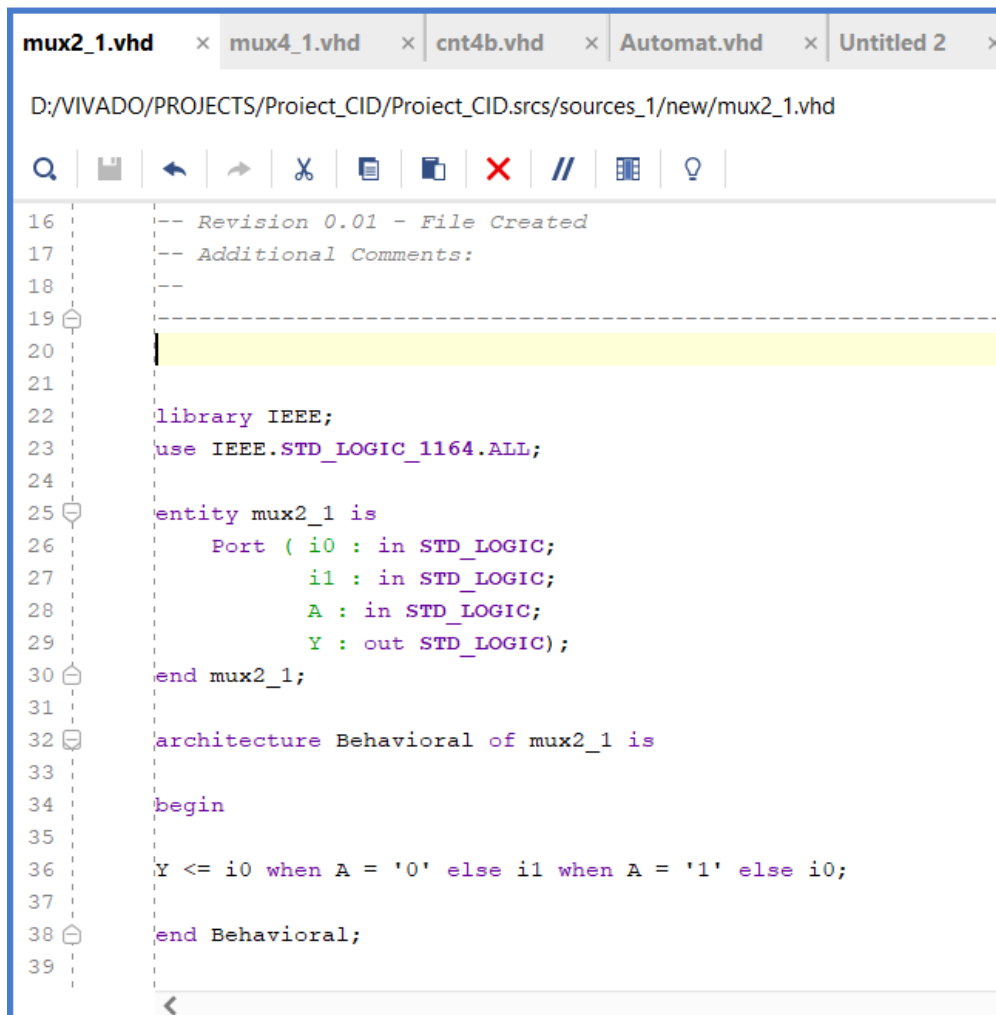

```
16      -- Revision 0.01 - File Created
17      -- Additional Comments:
18      --
19      -----
20
21
22      library IEEE;
23      use IEEE.STD_LOGIC_1164.ALL;
24
25      entity mux2_1 is
26          Port ( i0 : in STD_LOGIC;
27                i1 : in STD_LOGIC;
28                A  : in STD_LOGIC;
29                Y  : out STD_LOGIC);
30      end mux2_1;
31
32      architecture Behavioral of mux2_1 is
33
34      begin
35
36          Y <= i0 when A = '0' else i1 when A = '1' else i0;
37
38      end Behavioral;
39
```

## Mux4:1:

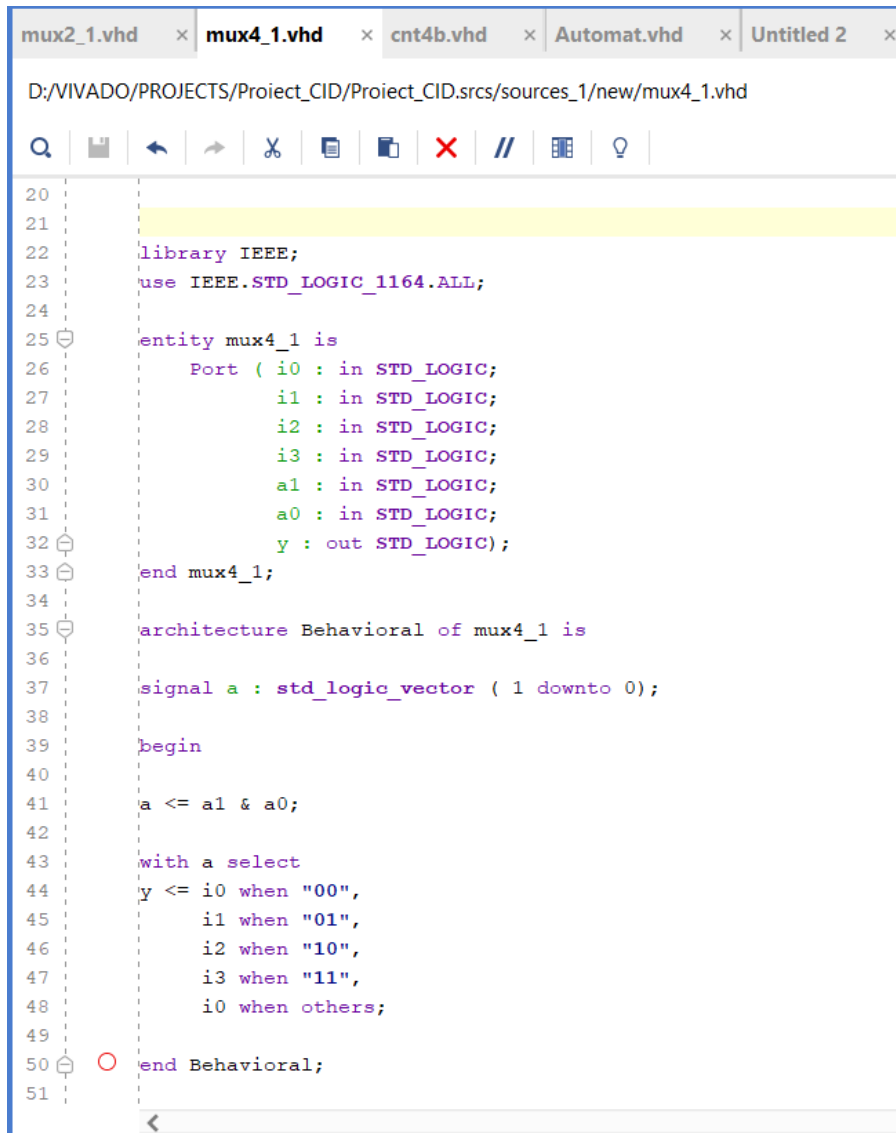

```
20
21
22 library IEEE;
23 use IEEE.STD_LOGIC_1164.ALL;
24
25 entity mux4_1 is
26     Port ( i0 : in STD_LOGIC;
27           i1 : in STD_LOGIC;
28           i2 : in STD_LOGIC;
29           i3 : in STD_LOGIC;
30           a1 : in STD_LOGIC;
31           a0 : in STD_LOGIC;
32           y : out STD_LOGIC);
33 end mux4_1;
34
35 architecture Behavioral of mux4_1 is
36
37     signal a : std_logic_vector ( 1 downto 0);
38
39     begin
40
41         a <= a1 & a0;
42
43         with a select
44         y <= i0 when "00",
45             i1 when "01",
46             i2 when "10",
47             i3 when "11",
48             i0 when others;
49
50     end Behavioral;
51
```

## Numarator 4biti:

```
mux2_1.vhd x mux4_1.vhd x cnt4b.vhd * x Automat.vhd x Untitled 2 x
D:/VIVADO/PROJECTS/Proiect_CID/Proiect_CID.srscs/sources_1/new/cnt4b.vhd
Q [ Save Undo Redo Cut Copy Paste Delete Comment Toggle Breakpoint Help
21
22 library IEEE;
23 use IEEE.STD_LOGIC_1164.ALL;
24 use ieee.std_logic_unsigned.all;
25 use ieee.std_logic_arith.all;
26
27 entity cnt4b is
28     Port ( d : in STD_LOGIC_VECTOR (3 downto 0);
29           clk : in STD_LOGIC;
30           r : in STD_LOGIC;
31           en : in STD_LOGIC;
32           ld : in STD_LOGIC;
33           q : out STD_LOGIC_VECTOR (3 downto 0);
34           cy : out STD_LOGIC);
35 end cnt4b;
36
37 architecture Behavioral of cnt4b is
38
39     signal qint : std_logic_vector (3 downto 0) := "0000";
40
41     begin
42
43         q <= qint;
44         cy <= '1' when (qint = "1111" and en = '1') else '0';
45
46         count4b: process(r, clk)
47         begin
48             if r = '0' then
49                 qint <= "0000";
50             elsif (falling_edge(clk) and ld = '1') then
51                 qint <= d;
52             elsif(falling_edge(clk) and ld = '0' and en = '0') then
53
54                 qint <= qint + 1;
55             else
56                 qint <= qint;
57             end if;
58         end process;
59     end Behavioral;
60
```

Automat:

Project Summary

Automat.vhd

D:/VIVADO/PROJECTS/Project\_CID/Project\_CID.srcs/sources\_1/new/Automat.vhd

Q

X

//

21

22 library IEEE;

23 use IEEE.STD\_LOGIC\_1164.ALL;

24

25 entity Automat is

26 Port ( r : in STD\_LOGIC;

27 clk : in STD\_LOGIC;

28 q : out STD\_LOGIC\_VECTOR (3 downto 0));

29 end Automat;

30

31 architecture Behavioral of Automat is

32

33 component cnt4b is

34 Port ( d : in STD\_LOGIC\_VECTOR (3 downto 0);

35 clk : in STD\_LOGIC;

36 r : in STD\_LOGIC;

37 en : in STD\_LOGIC;

38 ld : in STD\_LOGIC;

39 q : out STD\_LOGIC\_VECTOR (3 downto 0);

40 cy : out STD\_LOGIC);

41 end component cnt4b;

42

43 component mux2\_1 is

44 Port ( i0 : in STD\_LOGIC;

D:/VIVADO/PROJECTS/Proiect\_CID/Proiect\_CID.srscs/sources\_1/new/Automat.vhd



```
45         i1 : in STD_LOGIC;
46         A : in STD_LOGIC;
47         Y : out STD_LOGIC);
48 end component mux2_1;
49
50 component mux4_1 is
51     Port ( i0 : in STD_LOGIC;
52           i1 : in STD_LOGIC;
53           i2 : in STD_LOGIC;
54           i3 : in STD_LOGIC;
55           a1 : in STD_LOGIC;
56           a0 : in STD_LOGIC;
57           y : out STD_LOGIC);
58 end component mux4_1;
59
60 signal qint: std_logic_vector(3 downto 0);
61 signal en , ld : std_logic;
62 signal d: std_logic_vector (3 downto 0);
63 signal net1, q0_neg, q1_neg :std_logic;
64
65 begin
66
67 U: cnt4b port map ( d => d,
68                   clk => clk,
```


D:/VIVADO/PROJECTS/Proiect\_CID/Proiect\_CID.srscs/sources\_1/new/Automat.vhd



```
69             en => en,
70             r => r,
71             ld => ld,
72             q => qint);
73
74     q0_neg <= not qint(0);
75     q1_neg <= not qint(1);
76
77     U1: mux2_1 port map ( i0 => q0_neg,
78                           i1 => q1_neg,
79                           A => qint(2),
80                           Y => d(2));
81
82     U2: mux2_1 port map ( i0 => qint(2),
83                           i1 => '1',
84                           A => qint(2),
85                           Y => d(1));
86
87     U3: mux2_1 port map ( i0 => qint(1),
88                           i1 => qint(0),
89                           A => qint(2),
90                           Y => d(0));
91
92     U4: mux4_1 port map ( i0 => '1',
93                           --
94                           i1 => '1',
95                           i2 => '1',
96                           i3 => qint(0),
97                           a1 => qint(2),
98                           a0 => qint(1),
99                           y => ld);
100
101     en <= '0';
102     q <= qint;
103     d(3) <= '0';
104     end Behavioral;
```



## Sursa de simulare:

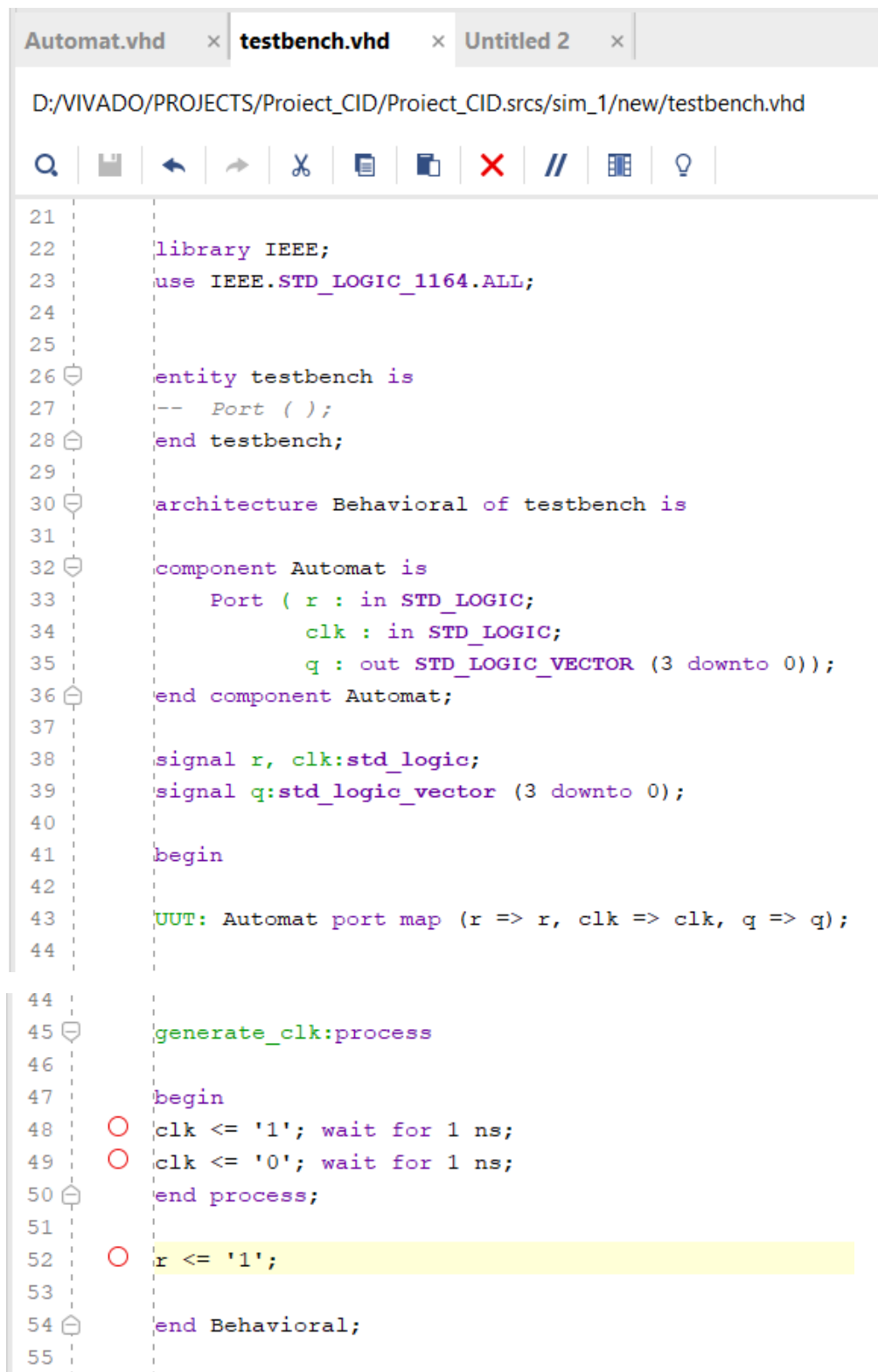

```
Automat.vhd x testbench.vhd x Untitled 2 x
D:/VIVADO/PROJECTS/Proiect_CID/Proiect_CID.srscs/sim_1/new/testbench.vhd

21
22 library IEEE;
23 use IEEE.STD_LOGIC_1164.ALL;
24
25
26 entity testbench is
27     -- Port ( );
28 end testbench;
29
30 architecture Behavioral of testbench is
31
32     component Automat is
33         Port ( r : in STD_LOGIC;
34               clk : in STD_LOGIC;
35               q : out STD_LOGIC_VECTOR (3 downto 0));
36     end component Automat;
37
38     signal r, clk:std_logic;
39     signal q:std_logic_vector (3 downto 0);
40
41     begin
42
43     UUT: Automat port map (r => r, clk => clk, q => q);
44
45
46
47 generate_clk:process
48     begin
49         clk <= '1'; wait for 1 ns;
50         clk <= '0'; wait for 1 ns;
51     end process;
52     r <= '1';
53
54 end Behavioral;
55
```

## Rezultatul simulării:

